

NEW POWER AMP MODULES

By Erno Borbely
Contributing Editor

Since I introduced the 60W amp in 1982, and the Servo-100 and DC-100 in 1984, a number of you who have built these amplifiers have given me some positive feedback. I have also received some comments and suggestions indicating there is room for improvement. So I have been continuously monitoring their performance and updating the designs.

I designed the original DC-100 with two pairs of output devices, addressing the more traditional speaker loads of 5–8Ω. Since many of you are using lower-impedance loads (some going as low as 1Ω), I have added higher-current devices to the output which allow loads in the 2–4Ω region. Due to the high supply voltage, a significant heatsink in-

crease is required to cope with the increased power dissipation. For high-current, low-impedance applications, the new power amp operates from a lower voltage than previous versions.

One problem with the old unit was the wiring of the TO-3 metal-can output devices. Although a pinout was published, it is easy to reverse a couple of

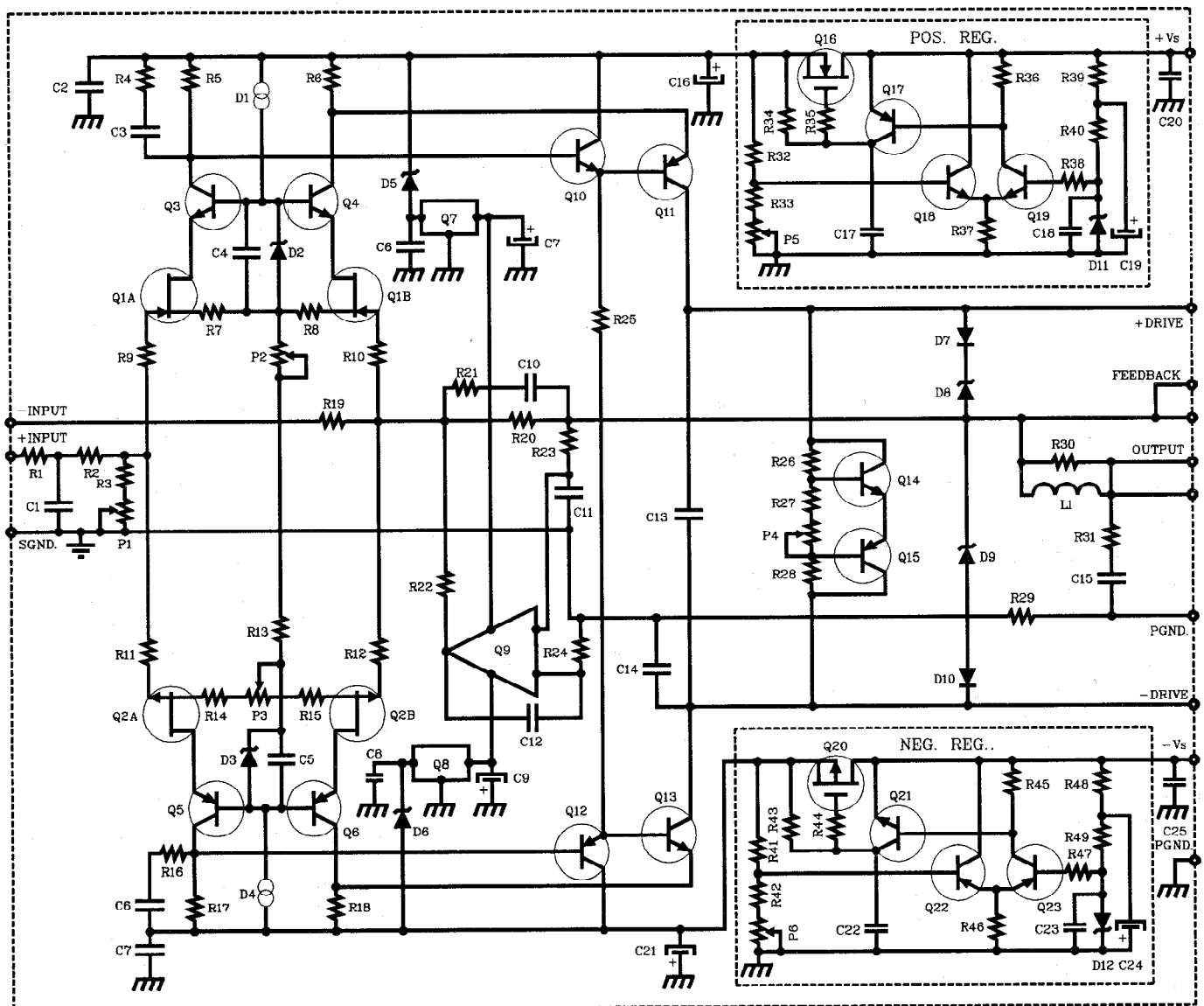


FIGURE 1: Servo-50 EB-691/125 driver board.

TABLE 1

TO-3P MOSFETs					
MOSFET PAIRS	PIN	D-S	I _D MAX	P _D	V _{GS(OFF)}
		Volt	Amp	Watt	Volt
2SK1058/2SJ162	GSD	160	7	100	0.15-1.45
2SK405/2SJ115	GDS	160	8	100	0.8-2.8
2SK1529/2SJ200	GDS	180	10	120	0.8-2.8
2SK1530/2SJ201	GDS	200	12	150	0.8-2.8
2SK414/2SJ119	GDS	160	8	100	2-5
2SK400/2SJ114	GDS	200	8	100	2-5
IRFP241/IRFP9241	GDS	150	12	150	2-4

Note: The first four types are especially suitable for audio use.

wires, which results in catastrophic failure. I have been monitoring the development of the TO-3P plastic package and believe they are now reliable enough for audio use. Different versions are available, making them suitable for

most applications. Plastic devices offer several advantages: they have only one hole and are easy to mount; when combined with specially designed output boards, the pin connections are practically fool-proof.

TABLE 2

EB-691/125 DRIVER BOARD PARTS LIST			
REF.	DESCRIPTION	REF.	DESCRIPTION
Capacitors			
C1	560pF/160V, PP, PS	Q12	2N5401
C2, 7, 13, 15	0.1µF/160V, PP	Q13	2SC2912 or 2SC3601
C3, 6	560pF/630V, PP, PS	Q14	MPSA06
C4-6, 8, 20, 25	0.1µF/100V, ceramic	Q15	MPSA56
C7, 9	10µF/35V, TA	D1, 4	40.2k resistor (when regulator) or J505, CR100/120, 1N5297 current diode
C10	56pF/630V, PP, PS	D2, 3	LM336Z-5.0
C11, 12	0.22µF/160V, PP	D5, 6	ZPY20, 20V/1W zener, without reg.
C14	330pF/630V, PP, PS	D7, 10	1N4148
C16, 21	47µF/63V, low ESR, ROE, EKR	D8, 9	ZPY15 or equivalent 1W zener
Output Coil			
L1	1.7µH (Int. diam.: 16 mm, length: 20 mm, wire diam.: 1.5-1.8 mm)	Trim pots	
Resistors			
R1, 7-12	100	P1	1k, P1 is used for balanced op.
R2	shorted	P2	200, multiturn cermet
R3, 22	100k (R3 = 499 for balanced operation)	P3	50, multiturn cermet
R4, 16	121	P4	5k (for 2SK405/2SJ115 "O"-type) 2k (for 2SK405/2SJ116 "Y"-type)
R5, 17	1.4k	Miscellaneous	
R6, 18	137	TO-92 heatsink for Q7, Q8	
R13	10	8-Pin DIL socket for Q9	
R14, 15	75	Heatsink for Q11, Q13, Q16, Q20, aluminum, 120 × 25 mm, 2-2.5 mm thickness	
R19	523 (for 26dB gain, single input) 1k (for balanced operation)	EB-691/125 PC board (120 × 120 mm)	
R20	10k/1.4W metal oxide	Solder pins	
R21	shorted	6.3 mm/1/4" flat connectors	
R23, 24	1M	Terminal blocks or eyelets for signal and power connection	
R25	22k/1.4W metal oxide	Note	
R26, 28	1.5k	All resistors 1%/0.5W metal film, ROE MK-2 or equiv.	
R27	681 (for 2SK405/2SJ115 "O"-type) 499 (for 2SK405/2SJ115 "Y"-type)	Positive and negative regulator	
R29	10/1.4W, metal oxide	R32, 41	10k/2W (22k in par. with 22k/1W)
R30	1/4.5W, metal oxide	R33, 34, 38,	1k
R31	10/4.5W, metal oxide	42, 43, 47	
Semiconductors			
Q1A, 1B	2SK389BL/V or 2SK240BL/V	R35, 44	100
Q2A, 2B	2SJ109BL/V or 2SJ75BL/V	R36, 45	681
Q3, 4	2SC3381GR/BL (MAT01, 2N2920, 2 × 2SC1775)	R37, 46	2.21k
Q5, 6	2SA1349GR/BL (MAT03, 2N3811, 2 × 2SA872)	R39, 40,	22.1k
Q7	78L15	48, 49	
Q8	79L15	P5, 6	1k, multiturn cermet
Q9	TL071, LF411CN or AD711JN	C18, 23	0.1µF/100V ceramic
Q10	2N5551	C19, 24	10µF/35V TA
Q11	2SA1210 or 2SA1407	C17, 22	560pF/100V ceramic
		Q16	2SK216
		Q17	MPSA56
		Q18, 19	2SC2240
		Q20	2SJ79
		Q21	MPSA06
		Q22, 23	2SA970
		D11, 12	LM336Z-5.0

An additional reason for designing the new modules was component availability. The NPD5566 and the AH5020CJ used in the DC-100's input stage, for example, were not available in Europe. This was alleviated when we began selling the kits, but in the meantime some components had been phased out of production.

I have recently introduced three new power amplifier modules: the Mini-Servo, the Servo-50, and the DC-102. Although sonically very similar, they have different applications. The Mini-Servo has relatively limited output power, and is ideal for active loud-speaker systems. The Servo-50 offers tremendous current capability, and will drive multiway passive as well as low-impedance ribbon speakers. The DC-102 is the favored driver for electrostatics. Both the Servo-50 and the DC-102 have the flexibility to drive any speaker given the right combination of power supplies and the appropriate number of output devices.

Servo Circuit

The Servo-50 is a high-current power amplifier, nominally rated at 50W into 8Ω. With a full complement of five output device pairs, it delivers 100W into 4Ω, and, depending on your power supply, close to 200W into 2Ω. It can drive a peak current of more than ±40A into 0.88Ω.

The 60W amp and the Servo-100 both use the same driver topology, with bipolar transistors in the input stage. Based on my experiences with the Class A preamp module ("Measuring Non-linear Distortions," TAA 3/90, p. 8), I selected its topology for the new servo driver circuit. The Mini-Servo and Servo-50 circuits are practically identical. [See Resource Box for details.--Ed.]

The Servo-50 driver schematic is shown in Fig. 1. I used either dual 2SK240BL/2SJ75BL or monolithic dual 2SK389BL/2SJ109BL Toshiba JFETs for the input devices, and monolithic dual 2SC3381GR/BL and 2SA1349GR/BL bipolar, low-noise transistors for the cascode input stage. Rated at 80V breakdown, they are suitable for most power amp inputs. I biased the cascode transistors with 5V reference diodes. These are floating with the Q1 and Q2 source voltage, which practically eliminates the voltage change across the input FETs and reduces the input capacitance to very low value. I set the input stage

current to 2mA with P2, and adjusted the input offset with P3.

The second stage, consisting of Q11 and Q13, is the well-known folded cascode circuit. As an extension of the input cascode circuit (through the use of resistors R8 and R18), it shows very good linearity; however, transistor selection is critical. Q11 and Q13 must have very low collector-base capacitance, low saturation voltage, and good linearity at the operating current. They must also have high breakdown voltage in order to cope with the high supply voltage.

I used BF757/760 video transistors in the original Servo-100 circuit. Some of these 300V devices have rather high saturation voltage at the 10–20mA operating current, but they will eventually be phased out of production. A TAA reader suggested I consider Sanyo's 2SC2912/2SA1210 video transistors, which are 200V devices in a TO-126 package with a rated collector current of 140mA and an f_T of 150MHz. They have extremely low collector-base capacitance and a reasonably good saturation voltage up to about 20mA collector current, making them ideal for the second stage.

TABLE 3			
EB-391/109 and EB-391/110 OUTPUT STAGE PARTS LIST			
REF.	DESCRIPTION	REF.	DESCRIPTION
Capacitors		Q8–12	2SJ162 Hitachi
C1–5, 8–12	0.1 μ F/100V, ceramic		2SJ115 Toshiba
C6, 7	100 μ F/63V low ESR, ROE, EKR		2SJ200 Toshiba
C13–17	33pF/100V, cog or dipped mica (Used only for 2SK1058/2SJ162 Hitachi MOSFETs.)	Miscellaneous	
Resistors		EB-391/109 PC board for B- and C-type (G-D-S pinout) MOSFETs	
R1, 2	100	EB-391/110 PC board for A-type (G-S-D pinout) MOSFETs	
R3–12	221	Solder pins	
R13	75/1W (for 2SK1058/2SJ162 MOSFETs) 150/1W (for 2SK405/2SJ115 "Y"-type)	6.3 mm/1/4" flat connectors	
Semiconductors		Terminal blocks or eyelets for signal and power connections	
Q1	2SK216	Notes	
Q2	2SJ79	All Components are mounted on the copper side.	
Q3–7	2SK1058 Hitachi (0.15–1.45V) 2SK405 Toshiba (0.8–2.8V) 2SK1529 Toshiba (0.8–2.8V)	In case the 2SK216/2SJ79 are mounted on the driver board, leave these and resistors R1, R2 and R13 out.	
		For stuffing the board without the drivers, see separate stuffing guide.	

Another complementary pair for this position is the 2SC3601/2SA1407, with an f_T of 400MHz. The second-stage bias transistors, Q10 and Q12, are TO-92 high-voltage devices for which I am using the 2N5551/2N5401.

Q14/Q15 serve as a complementary V_{BE} multiplier for biasing the output stage. I selected this dual-transistor ver-

sion because of the relatively high bias needs of some of the output MOSFETs.

Driver Boardom

I mounted the source follower drivers on the output board rather than on the driver board for several reasons, the simplest being that I didn't have room for them on the driver board. More im-

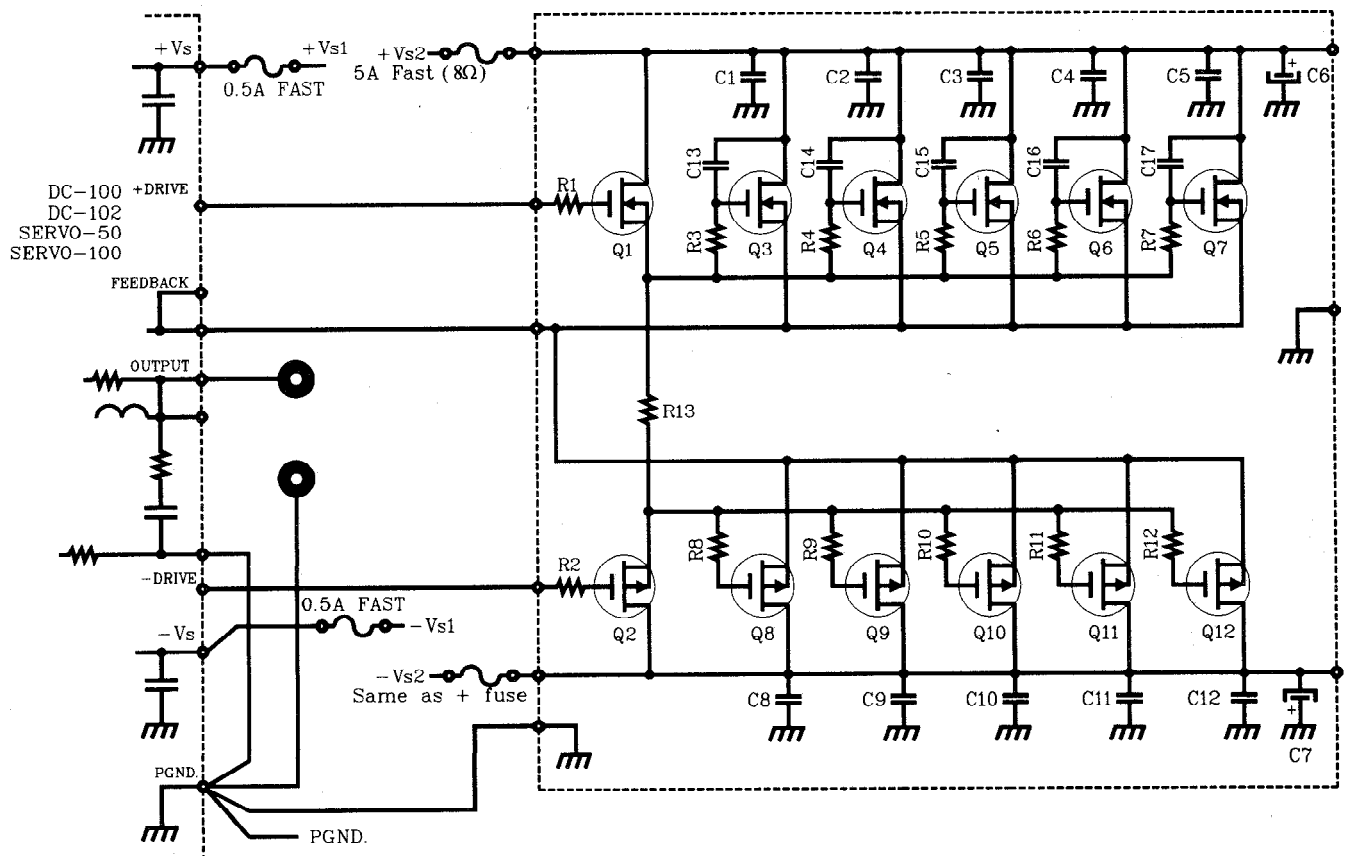


FIGURE 2: High-current output stage (EB-391/109 or EB-391/110). When the 2SK216/2SJ79 drivers are mounted on the driver board, remove Q1, Q2, R1, R2, and R13.

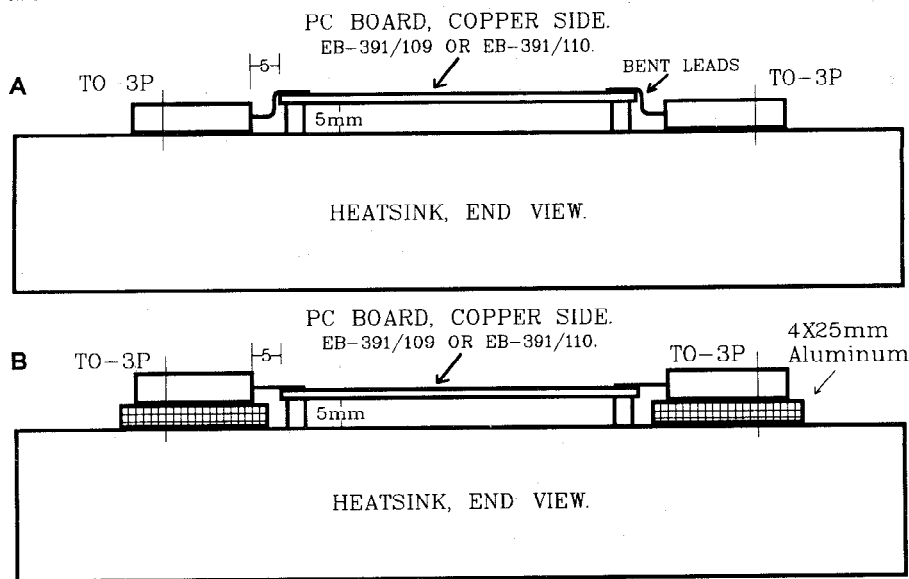


FIGURE 3A: Transistors mounted directly on heatsink. **B:** Transistors mounted with straight legs on 4 x 25 mm aluminum. Note: Aluminum and heatsink must be flat for good thermal contact.

portantly, mounting them as I did reduces the distance between the driver and output transistors, which in turn reduces the risk of high-frequency oscillations. The third reason is thermal stability. Some of the output MOSFETs have positive temperature coefficients, while the 2SK216/2SJ79 drivers have negative temperature coefficient when operated above 20mA drain current. Mounted on the same heatsink, they tend to compensate each other. Finally, you can run the drivers at higher current for improved linearity without heatsinking problems.

The Servo-50, Mini-Servo, and DC-102 driver circuits have high open-loop gains in the order of 85-90dB, with an open-loop frequency response of about 2kHz. The Class A topology with a source follower output results in a second stage with very little loading (only the source followers' input capacitance), and consequently high gain. The advantage of high gain and plenty of feedback at midfrequencies is that they reduce the by-products of nonlinearities which are outside the audio band.

You can reduce the open-loop (OL) gain by loading the second stage. For example, two 100k resistors connected from the second stage collectors (one from each side of the bias circuit for symmetry) will reduce the OL gain to about 70dB and increase the OL frequency response to close to 20kHz. Increasing the input stage source resistors will further reduce the gain. (I have not been able to verify the sonic advantages

of these modifications, and so have not included them in my designs; however, please try them and report the results.)

Theoretically, the Servo-50 is a DC-coupled amplifier. JFETs have a much higher temperature drift than bipolars, however, and this causes DC offset. If you are running your amp at a constant (and relatively low) temperature, simply trim the DC offset to zero with P3. If the temperature range is expected to vary widely, I recommend installing servo amp Q9, which is supplied with $\pm 15V$ by Q7 and Q8. D5 and D6 are connected in series with Q7 and Q8 to protect them from input/output (I/O) overvoltage, although they are unnecessary if the supply voltage across C16 and C21 is less than or equal to $\pm 50V$.

Driver circuits can benefit from regulated supplies, although I am not con-

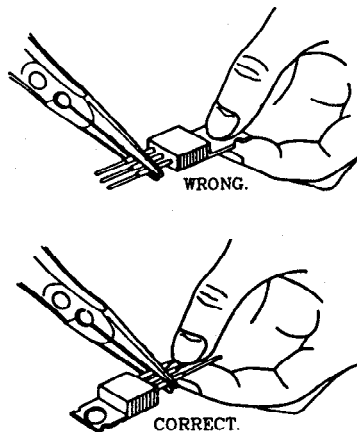


FIGURE 4: Bending transistor leads.

vinced that the output stages need them. "Pos. Reg." and "Neg. Reg." in Fig. 1 are discrete regulators comprised of a differential input stage, a driver, and a MOSFET output stage. The MOSFET and Q11/Q13 second-stage transistors are mounted on the same heatsink. The reference voltage is supplied from D11 and D12, which are LM336Z-5.0 reference diodes. P5/P6 trim pots in the feedback circuit adjust the output voltage over a 35-50V range.

The input voltage to the regulator must be a minimum of 5V higher than the output voltage. Thus, the regulated supply voltage requirements are: regulated output supply for the drivers of $\pm 45V$ ($\pm 40V$ output voltage plus 5V) and $\pm 50V$ input voltage ($\pm 45V$ plus 5V). I recommend operating the regulators with $\pm 55V$ input voltage and adjusting the regulated voltage to $\pm 45-48V$. Due to circuit simplicity, the regulators are not short-circuit proof, but they tolerate higher I/O voltage differences than IC regulators.

The generous-sized output pads on the PC board offer a number of connection possibilities: $\frac{1}{4}$ " Quick Connect connectors; the dual, screw-type terminal blocks with 5 mm or 0.2" pin spacing; or normal solder pins. You can also solder your cable directly to the board.

Resistors Reduplicated

Feedback resistor R19 appears twice in the stuffing guide. If you use the amp with single input, the 523W resistor should be mounted in the R19 (1) position. For use with balanced inputs, install the 1.1k resistor where R19 (2) is shown. Obviously, both can be mounted, but only one can be active at a time. The heatsink for second-stage transistors Q11/Q13 and regulator transistors Q16/Q20 is 120 x 25 x 2 mm aluminum.

I suggest you begin the board assembly by testing and adjusting the two regulators. First, place the common heatsink of Q11, Q13, Q16 and Q20 on the board, then mount pass transistors Q16 and Q20 on the heatsink.

With the positive regulator components in place, connect a 470 Ω /5-10W resistor across C2 or C16, and a voltmeter across the resistor. Apply +55V unregulated voltage to +Vs. Depending on P5's position, the output voltage should be between 30-55V. Adjust the regulated voltage to +45V with P5, then disconnect the load resistor and recheck the voltage. The same reading should ap-

Continued on page 15

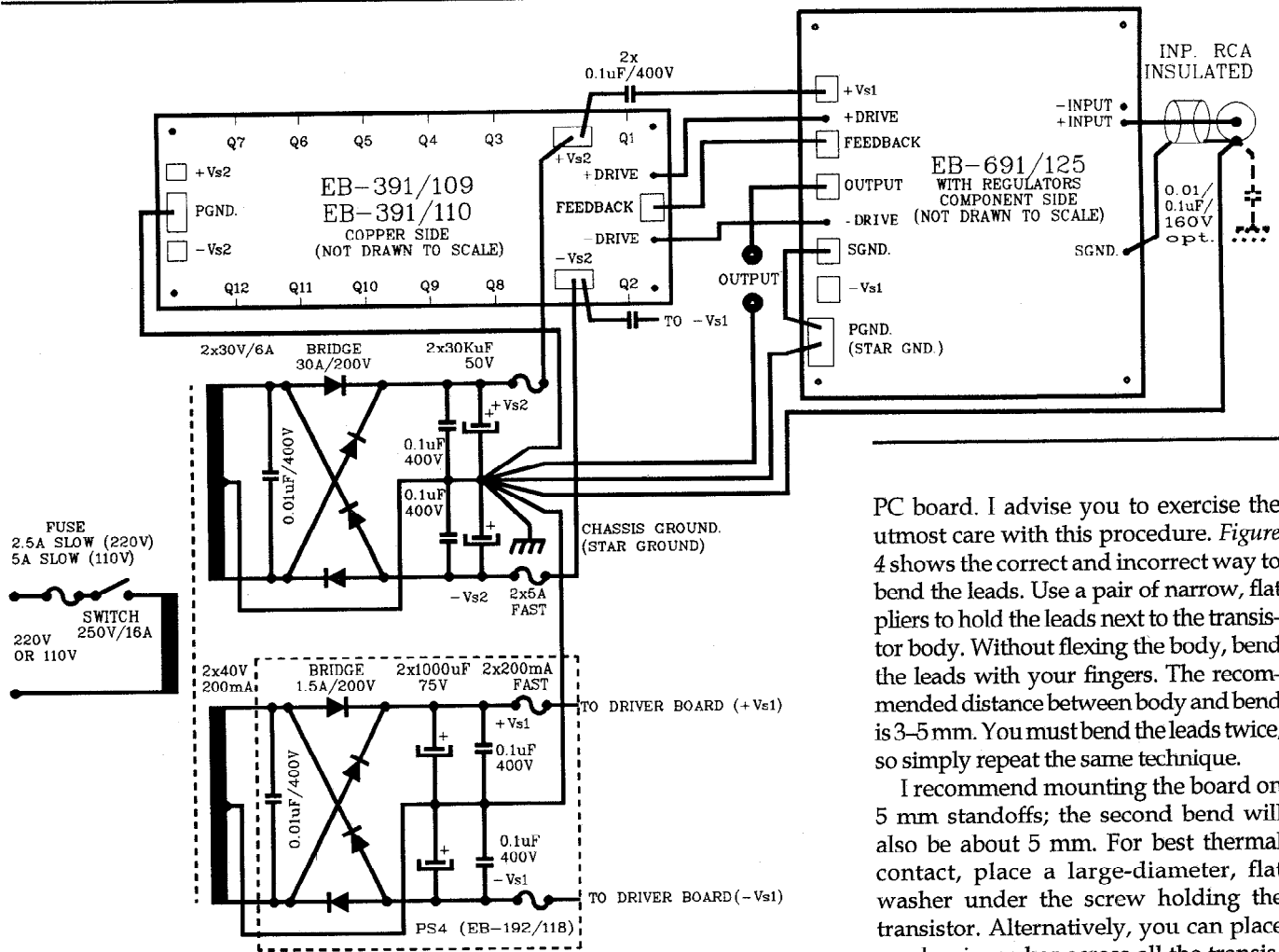


FIGURE 5: Proposed wiring diagram for monoblock with dual power supply.

Continued from page 12
 pear between the loaded and unloaded voltage on a 3½-digit DVM set to 200V.
 If you can't adjust the voltage, or if the difference is greater than 0.1V, recheck all components for correct placement/orientation. Set your scope on AC and the highest possible sensitivity. Connect it across the load resistor and check for output oscillation. When you have mounted all of the negative regulator components, repeat this procedure. You can then assemble the components on the board. Mount the output coil last, as some of the components are mounted partially under it. Make certain that the four heatsink transistors are insulated with mica, or the newer inert plastic isolators.

Prepare to Mount
 The EB-391/109 and 110 output boards (and their mini companion, the EB-792/111) have been developed for output stages using TO-3P output devices. The two versions have two different pin

configurations: G-D-S for the 109 and 111, and G-S-D for the 110. The boards also incorporate the 2SK216/2SJ79 drivers, enabling you to mount them on the main heatsink with the output MOSFETs. (If the drivers are mounted on the driver board, you can leave them out.) The output stage schematic is shown in Fig. 2.
 The TO-3P devices bolt directly onto the heatsink with single-hole mounting. Transistor connections are facilitated by the special PC boards, to which all transistors are soldered. Since the PC board must be mounted off the heatsink to avoid short circuits, the transistors will be at a different level (Fig. 3a). You can build a pedestal using an appropriate aluminum profile to raise the transistors (Fig. 3b), although this method introduces an extra thermal resistance between the transistors and the heatsink. It should therefore be used only when necessary.
 If you mount the transistors directly onto the heatsink, you must bend the leads before you can solder them to the

PC board. I advise you to exercise the utmost care with this procedure. Figure 4 shows the correct and incorrect way to bend the leads. Use a pair of narrow, flat pliers to hold the leads next to the transistor body. Without flexing the body, bend the leads with your fingers. The recommended distance between body and bend is 3-5 mm. You must bend the leads twice, so simply repeat the same technique.

I recommend mounting the board on 5 mm standoffs; the second bend will also be about 5 mm. For best thermal contact, place a large-diameter, flat washer under the screw holding the transistor. Alternatively, you can place an aluminum bar across all the transistors and use the individual screws to tighten the bar (and, consequently, the transistors). Use an insulator and a generous amount of silicone grease under each transistor.

Table 1 lists some available TO-3P MOSFETs. The Hitachi 2SK1058/2SJ162 are the plastic equivalents of the well-known 2SK135/2SK50 TO-3 metal cans. Their positive and negative temperature coefficient crossover point is around 100mA, with no thermal runaway if you operate them at higher drain current. The Toshiba 2SK405/2SJ115 have a much higher crossover point and good thermal stability, provided you use the Hitachi 2SK216/2SJ79 drivers mounted on the main heatsink with the output devices.

The 2SK1529/2SJ200 are recommended for very-high-power amplifiers. They have positive temperature coefficient across the entire current range and require special care to ensure thermal stability.¹

The last three MOSFET pairs are also suitable for audio applications. Their primary difference is a significantly

Resources For This Article

Please contact the following companies for pricing and other information as shown:

Old Colony Sound Lab, PO Box 243, Dept. A93, Peterborough NH 03458, (603) 924-6371, (603) 924-6526; FAX (603) 924-9467 (24 hours).

1. PC boards only (less components):

Servo-50 (EB-691/125)
 DC-102 (EB-1091/117)
 Output without Drivers (EB-391/110)
 DC Protection (EB-192/132)

Welborne Labs, 971 E. Garden Dr., PO Box 260198, Littleton CO 80126-0198; (303) 470-6585; FAX (303) 791-7856.

1. Information about the Mini-Servo and the DC-150.

2. PC boards and/or kits:

Mini-Servo (EB-692/116)
 Little Output with Drivers (EB-792/111)
 Output with Drivers (EB-391/109)
 DC-150 (EB-892/127)

Borbely Audio, Melchior Fanger Strasse 34A, 82205 Neu-Gilching, Federal Republic of Germany; 011-49-8105-5291; FAX 011-49-8105-24605 (24 hours).

1. PC boards and/or kits:

All of the above except Mini-Servo, Little Output, and DC-150.

For those interested in fabricating their own boards, prints of all board patterns and stuffing guides are available on request. Please send a 9" x 12" manilla SASE with postage for 2 oz. (international readers, please include postal coupons) to: TAA, PO Box 576, Dept. EB393, Peterborough, NH 03458-0576.

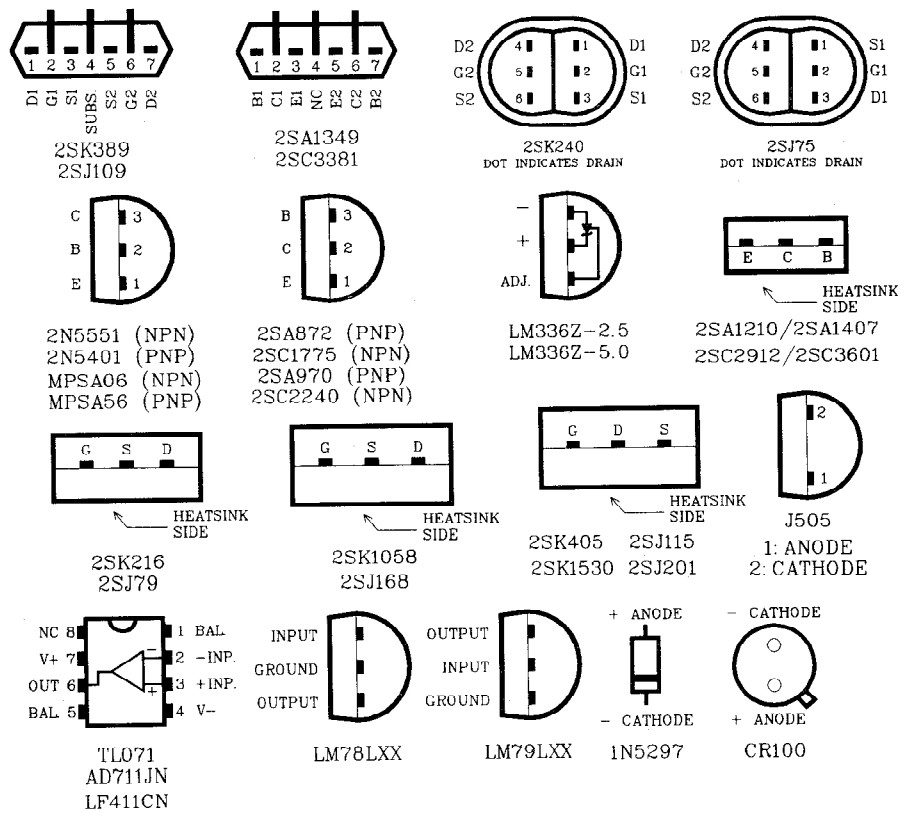


FIGURE 8: Pin configurations for Servo-50 devices. Note: All devices shown bottom view.

mal overload, and the amplifiers will not survive any long-term short at the output. If you expect to encounter short circuits, especially in the testing phase, you should use 10V zeners for current limiting and 2A fast fuses for the plus/minus supplies. Once everything is in working

order, you can make adjustments for your particular load condition.

Set-Up Procedure

You should invest in a variable transformer before you start this procedure; a 500VA Variac™ should be adequate. It can save you some expensive output devices, not to mention the aggravation

of replacing blown transistors and other components.

Before turning on the AC power, place P2 and P4 in their maximum-resistance positions and P3 in midposition. Don't install Q9 if it is socketed. If you have an 8Ω load resistor with a minimum rating of 50W, connect it to the

Continued on page 19

1993 Design Manual and Catalog

Our 1993 160+ page Design Manual and Catalog is loaded with parts, kits, schematics, books, software, and how-to instructions for building and modifying high quality solid state and vacuum tube audio equipment. For your copy send \$10 (United States and Canada), or \$14 (International).

PH: 303-470-6585 (evenings best)
 Fax: 303-791-7856 (24hrs)

We Now Accept Visa and MasterCard



1993 Product Offerings

MIT MultiCap™ Capacitors
 Kimber Kable OFC/Silver Hookup Wire
 Caddock Resistors
 Strongbox and other Enclosures
 Vampire OFC RCA Jacks
 Tesla EL-34 Power Tubes
 MagneQuest™ Output Transformers
 Analog Devices & Linear Technology Semi's
 Largest Selection of WIMA Caps (over 50 values)
 Plus: qwik cad pcb software-Version 4.0 (free demo disk included with catalog), TEC-200 Film
 Siemens caps, Roederstein resistors/caps, Wonder Caps-Wire-Solder, WBT, Vampire, Neutrik, Ram Labs, Audiovalve, Grayhill, Bourns, TKD, Toshiba
 Hitachi, Caig Laboratories-ProGold and much more

Kits Available in 1993

Tube:

35 and 60 watt Amplifiers (mu-stage design)
 Dynaco ST-70/MKIII Mods
 Line and Phono Preamps (hybrid mu-stage)

Solid State:

Borbely Mini-Servo 60 W Amp
 Borbely DC-150 150 W Amp
 Borbely New Class-A Line Amplifier
 Unity Gain Buffer Stage
 Several Regulated Power Supplies

Passive:

Passive Linestages
 Stepped Attenuators

Welborne Labs
 audiocraft design
 p.o. box 260198, littleton, co usa 80126-0198

supplies

service

Audio Amateur Back Issues continued

1986 Electronic Turntable Speed Control • Cable-ready and Stereo TV • Borbely Preamp (Part 2) • Three-Channel Stereo • 20W Class A Amp • Solid-state Relay Power Control • 10x Instrumentation Amp • Vacuum Tube Primer (Part 1) • Op Amps for CD Players • Yamaha CD2 Mods • Hafler DH-100 Mods • Signal Sniffer • Borbely Moving Coil Preamp (Part 1) • 500W MOSFET Power Amp (Part 1) • Dyna FM-3 Mod • Frequency Multiplier • Grid Isolation Resistors •

1987 Borbely Moving Coil Preamp (Part 2) • Decca Records Montreal Symphony's Petrushka • 500W MOSFET Power Amp (Part 2) • Wideband Power Supply • Improve Logical Systems' 1081 Analyzer • Connectors (Parts 1, 2) • Digital Tape Dropout Detector • Pulse Code Modulation Update • Crowbar Protection for Power Supplies • Plate Reverb Theory • Vacuum Tube Primer (Part 2) • The Nature of Sound (Parts 1, 2) • The Aurora: Cleveland PAS Preamp • Vacuum Tube Heater Regulator • Mr. Bill Turntable • CD Player Group Delay Problems Analyzed • Oscilloscope Upgrade (Part 1) • Power Supply Inductance • Construct Hafler's XL-10 A/B/D Distortion Test Box •

1988 POGGE-4: Philips/Magnavox CD Mods (Parts 1, 2) • Audio Power Meter • New Buffer • Push/Pull Shunt Regulator • Oscilloscope Upgrade (Part 2) • 40W All-MOSFET Power Amp • Audio System Design Procedures • Sequenced Power Switch • Switchless Audio Switch • Tape Timing Control • Hafler DH-330 Mod • Belt Drive Turntable Revisited • Car MOSFET Amp (Part 1) • Magnavox 14-bit CD Mods • A. Sugden Profile • AC Motor Stabilizer • Computer Programs for Stepped Volume Controls •

1989 Apple II CD Player Control • DC300B Tube MOSFET 150W/Channel (Parts 1, 2) • Car MOSFET Amp (Part 2) • Marsh Preamp Mod • Direct Mods for Magnavox CEDB-580 CD Player • Multi-tone Distortion Measurement (Parts 1, 2) • Tape Calibration Oscillator • Simple CD Output Amp • AC Sensing Control • Digital Gain Control Theory • Ford Auto Electronics Upgrade • Design Stepped Volume Controls • 14-bit Magnavox CD Players Update • Feedforward Error Cancellation • Dyna PAT-4 Redesign • ADCOM GFA-555 Power Supply Regulator •

1990 MOS Preamp (Parts 1, 2) • Tigersaurus Restoration Odyssey (Parts 1, 2) • A Biology of Music • High Performance Analog Circuitry for CD Players • Understanding RIAA Curves • Multi-tone Distortion Measurement (Part 3) • Power Pro Failsafe Line Protection • Modify Crown's IC-150 Preamp • Auditory Perception • Balanced Line Design • Audio Engineering Careers • Simple Curve Tracer (Part 1) • Build a Digital Level Control • Parallel Audio Regulators • Amp Protection Circuit •

1991 Improve the CDB-650's DAC • Balancing Amps • Active Inverse RIAA Circuit • Simple Curve Tracer (Part 2) • Dalzell on Noise • Electrostatic Headphone Amp • Remote Control Volume/Balance System • Borbely Preamp: The Modules • Heath's IG-72 Sine Wave Generator • Ground Loops Revisited • Phase Coherent Cable • Stepped Attenuator for Balanced Audio Amps • New Control Preamp (Part 1) • IR Remote Slave • Improve Your Power Supply • Build a Video Test Generator •

1992 Salvaged 35W Power Amp • New Control Preamp (Part 2) • Centralized Power Conditioner • POGGE-5: DAC960 Rite of Passage (Parts 1, 2) • Build an A-Weighting Filter • Safe Soldering • Balancing Differential Circuits • Balanced-Jack Differential Audio Project • MOSFET Dyna ST-120 Mod • Pots: Encapsulated Modules • Build the A75 Power Amp (Part 1) • Anti-shock Turntable Cradle • High-Quality AM from Crystal Radio •

Continued from page 17

output. Connect the minus and plus inputs to signal ground at the input. Remove one of the output stage supply fuses and connect an ammeter set to 0.5 or 1A across it. If you have a scope and a DC voltmeter, connect both to the output. Slowly turn on the AC power using the Variac. The current measured by the ammeter should not exceed a few hundred milliamps, and the DC voltage at the output should remain around 0V.

Connect the DC voltmeter across resistor R5 (or R17) and adjust the input stage current to approximately 2mA, which will produce a voltage drop across the resistors of 2.8V. If you are lower than 2.8V, short R13. If you are higher, increase R13's value to 200W. (This might be necessary if you are using "V"-type input devices.) Reconnect the DC voltmeter to the output and try to adjust the DC offset to 0V. You might have difficulty with this if you are using high-bias output transistors which are completely off. In this case, leave the offset for the time being and adjust the bias.

Monitoring the current through the output transistors with the ammeter, initially adjust the bias to approximately 500mA. Now return to the DC offset at the output and adjust it as close as possible to 0V with P3. As shown on the schematic, this is actually a DC amplifier, and it can be used as such provided the input FET's ambient temperature doesn't change more than 10–20°C. As FETs drift more with temperature than bipolar transistors, you should always use the servo in high-temperature environments. Switch off your amp and install Q9. With the servo installed, the output offset should be less than a couple of millivolts.

Once you have made the basic DC adjustments, remove the short from the plus input and connect a 1kHz/0.5V RMS signal to it. Turn on the amplifier and observe the output with a scope. It should be an undistorted sine wave, with no high-frequency oscillation. If you have a total harmonic distortion (THD) analyzer, perform the usual measurements at different frequencies.

When the amp is running properly, connect it to your system. To get the best

Continued on page 41

Reference


1. *Mospower Applications*, "Temperature Compensated Biasing for Power MOSFETs in Linear Amplifiers" (Siliconix, 1984): 5–14.

SpeakerBuilder

THE LOUDSPEAKER JOURNAL

The magazine
that finally deals seriously with
the art and craft of speaker building

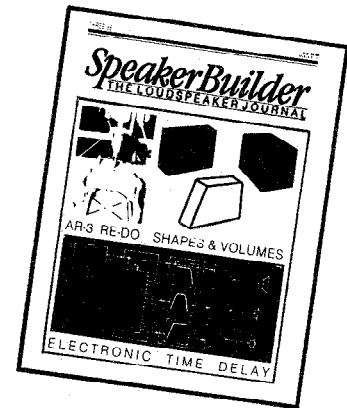The *Art* of building a speaker is to optimize that mixture of design and engineering to balance all the parameters for the most beautiful sound possible. The *Craft* is knowing how and why. **Speaker Builder** gives you knowledge—from driver parameters and crossovers to woodworking—to develop and refine your techniques, and to get the most out of your system.



Speaker Builder helps you explore new designs with how-to construction articles, and can show you how to modify your old speakers and make them sound better than ever. Learn from our writers who turn abstract theory into practical approaches, and from the experience of other readers who have been down the road before you. **Speaker Builder** is the best investment you can make in your system—six issues per year filled with stimulating and exciting ideas.

YES, Sign me up!

Two years @ \$45 (12 issues)

One year @ \$25 (6 issues)

Canada add \$6 per year postage.

Remit in US \$ drawn on a US bank.

NAME _____

STREET & NO. _____

CITY _____

STATE _____

ZIP _____

MC OR VISA NUMBER _____

EXPIRE _____

Speaker Builder

PO Box 494, Dept. A93

Peterborough, NH 03458-0494

(603) 924-9464 FAX: (603) 924-9467

Answering machine for credit card orders only:
before 9:00 a.m., after 4:00 p.m. and weekends.
Have all information plus MC/VISA available.

Contributing Editor Erno Borbely responds:

You might have an RF oscillation in your amp. Connect an oscilloscope to the output and you should be able to detect any RF oscillation.

□

POWER AMP MODULES

Continued from page 19

sound, you must experiment with the bias. Adjust it to 100–200mA per pair of output devices if you are using large heatsinks. With a full complement of output devices, the total bias current can be in excess of 1A.

If the supply voltage on the output devices is approximately $\pm 40V$, the total dissipation is a minimum of 80W, requiring a heatsink with a 0.25–0.3°C/W thermal resistance at 25°C ambient temperature. The SK-56 heatsink shown in Fig. 7 is sufficient for approximately 80W dissipation with proper air circulation. I recommend using a thermal breaker with a 70°C cut-out temperature on the heatsink.

□

THE HEAT'S OFF

Continued from page 29

even though you used a new breed of thermal pad and a large heatsink, you can only safely dissipate 52.1W with this thermal design. And despite the fact that it's rated at 100W!

The example illustrates how simple it is to analyze a thermal circuit. All you need is an understanding of the heat transfer modes and appropriate information on the components used to transfer the heat. Implementing proper thermal design techniques will result in a high level of reliability and save time, trouble, and money.

□

Ask TAA

Continued from page 36

optimum performance. After aligning a playback head, I usually check the phase at several frequencies between 1–15kHz. If the phase relationship between the left and right channels varies with frequency, it is indicative of the equalization phenomenon you described. Thanks for sharing this extremely prudent advice with us.

□

MONARCHY AUDIO
DT-40A is born

\$1499—factory direct

- * Ultra-stable Audio/Video Transport
- * Jitter-free Re-clocking Circuitry
- * RCA and Balanced Digital Outputs

SPECIAL INCENTIVES
OFFERED EXCLUSIVELY
TO TAA READERS.

CALL OR WRITE TO GET FULL DETAILS.
INDICATE YOUR ACCOUNT NUMBER.

MONARCHY AUDIO

380 SWIFT AVE. UNIT # 21
S. SAN FRANCISCO, CA 94080
TEL: (415)873-3055
FAX: (415)588-0335

Fast Reply #CH52

42,398

ELECTRONIC COMPONENTS

Whether you order 1 part or all 42,398...MOUSER stocks and...ships same day!!

CALL...
(800) 992-9943

for your
FREE CATALOG

2401 Hwy 287 N.
Mansfield, TX 76063

MOUSER[®]

ELECTRONICS

Sales & Stocking Locations Nationwide

Fast Reply #CH181